

QRP-RIG


Arduino based SDR RX & TX

QRP-RIG

- Objective is to build a QRP, SDR based, RX & TX on an Arduino Shield
- Wide band operation, external BPF to cover 40, 30 & 20m
- All modes supported by HDSDR software (PC or Mac)
- Based on principles in ARRL article “Software Defined Radio for the Masses”, original of Flexradio designs.

QRP-RIG


Transmitter

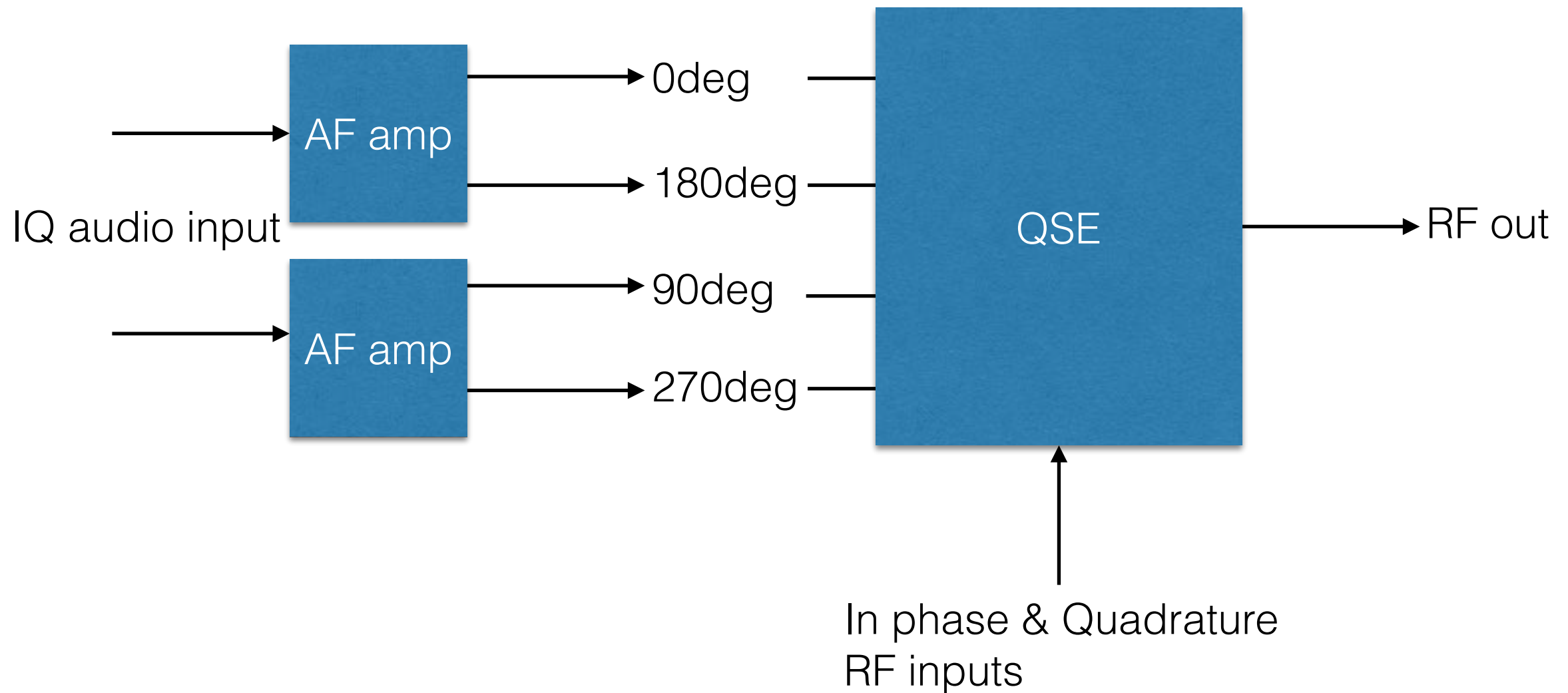

QSE = Quadrature Sampling Exciter

QRP-RIG

Receiver

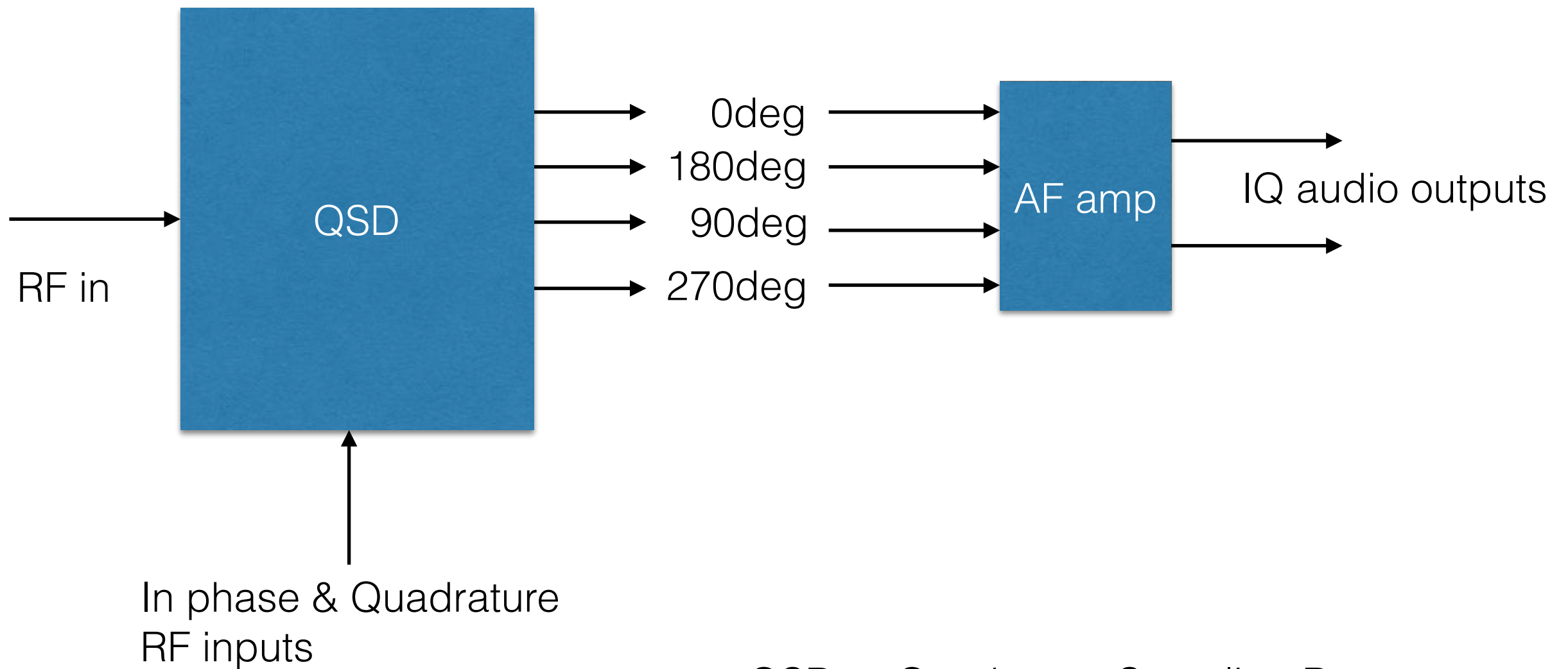

QSD = Quadrature Sampling Detector

Choice of ICs


- Mixer must have low R_{on} and high speeds (needs to switch at 14MHz (20m)).
 - FST3253 is the choice
- Audio amps need low noise, balanced inputs for RX, and low output impedance to drive the TX mixer
 - Ideal part is the relatively unknown SSM2135
Dual op-amp

ICs


Mixer

Dual mixer, so can use balanced input

Logic Diagram

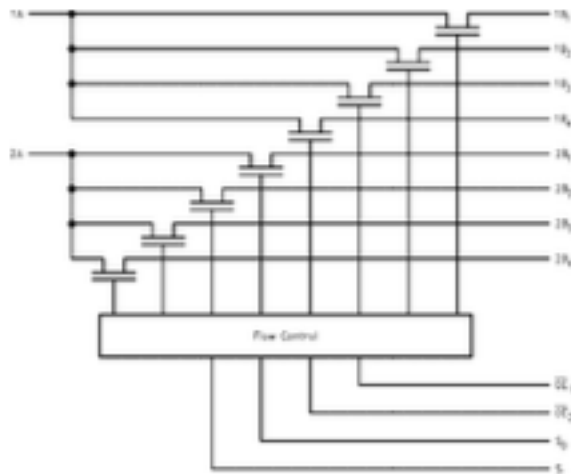

Connection Diagram

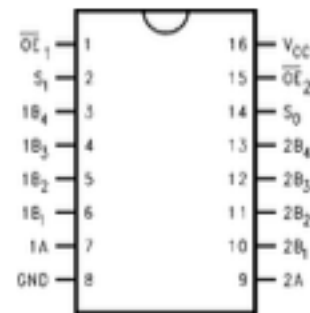

Truth Table

S ₁	S ₀	OE ₁	OE ₂	Function
X	X	H	X	Disconnect 1A
X	X	X	H	Disconnect 2A
L	L	L	L	A = B ₁
L	H	L	L	A = B ₂
H	L	L	L	A = B ₃
H	H	L	L	A = B ₄

Pin Descriptions

Pin Name	Description
OE ₁ , OE ₂	Bus Switch Enables
S ₀ , S ₁	Select Inputs
A	Bus A
B ₁ , B ₂ , B ₃ , B ₄	Bus B

Op-amps

Dual op-amps. Use 2 for TX, one for RX

PIN CONNECTIONS

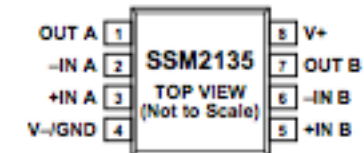


Figure 1. 8-Lead Narrow Body SOIC (R Suffix)

FUNCTIONAL BLOCK DIAGRAM


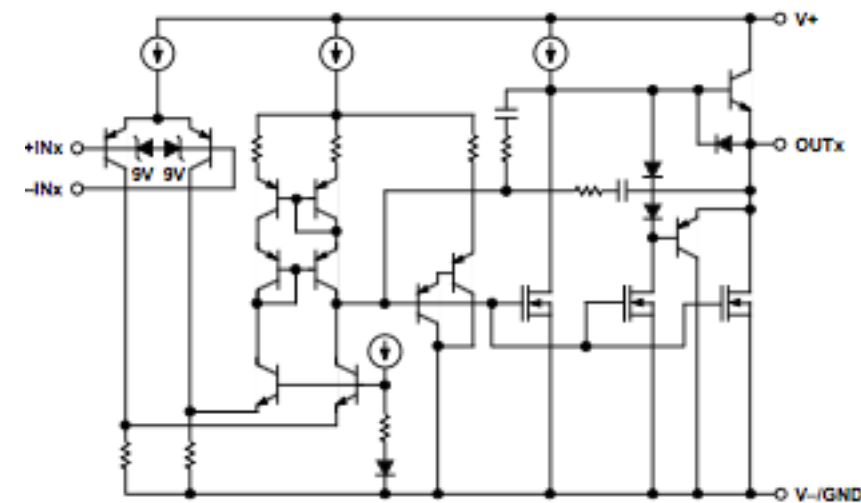


Figure 2.

Surface mount devices save space on PCB


Circuit details

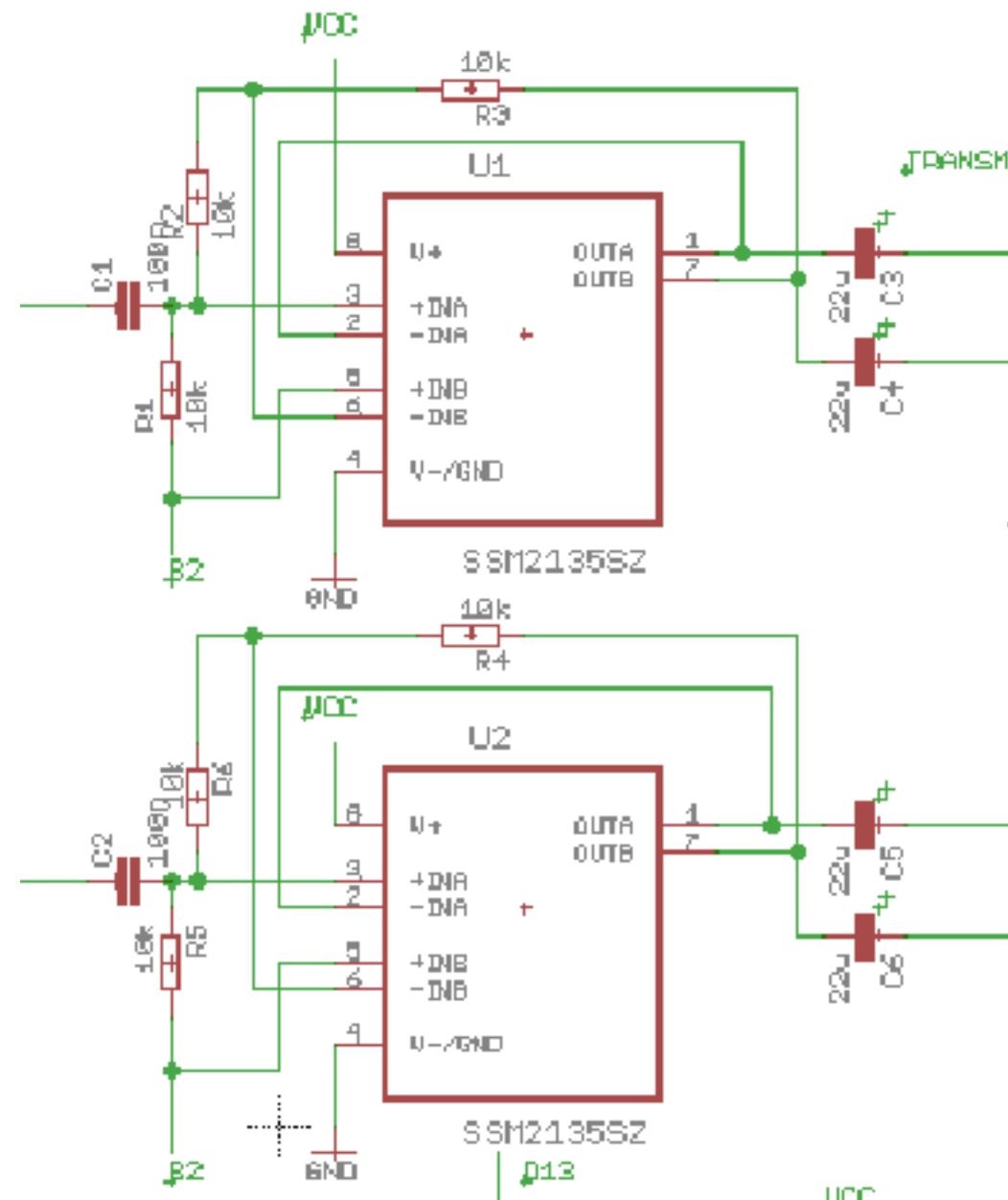- TX amplifiers.
- Each SSM2135 has
 - 0 and 180deg outputs
 - 90 and 270deg outputsfrom I & Q audio inputs
- Able to drive $>2V_{p-p}$ into 50R loads



Circuit details

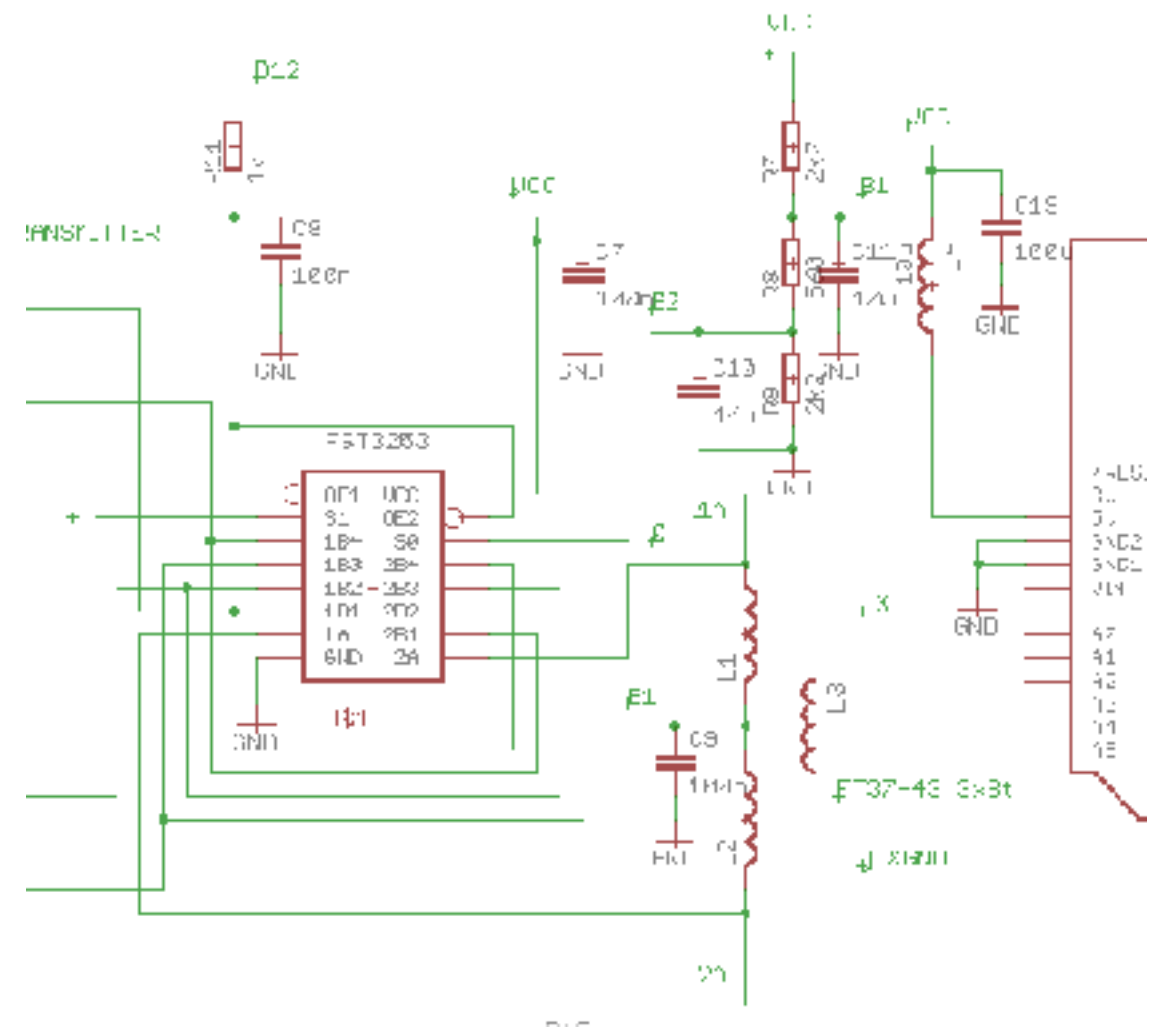- TX Mixer
 - Balanced transformer output 50+50R impedance
 - I&Q phase RF switch inputs from DDS
- BIAS provided at B1=2.5V for mixer, B2=2V for op-amps



Circuit details


- RX Mixer
 - Inputs in parallel with TX, only one active at a time!
 - Filter caps give > 48kHz bandwidth (+/-48kHz tuning range, for 96kHz ADC)

$$BW = 1/n * \pi * R * C$$

n = 2 for balanced input


R = 50R

C = 47nF

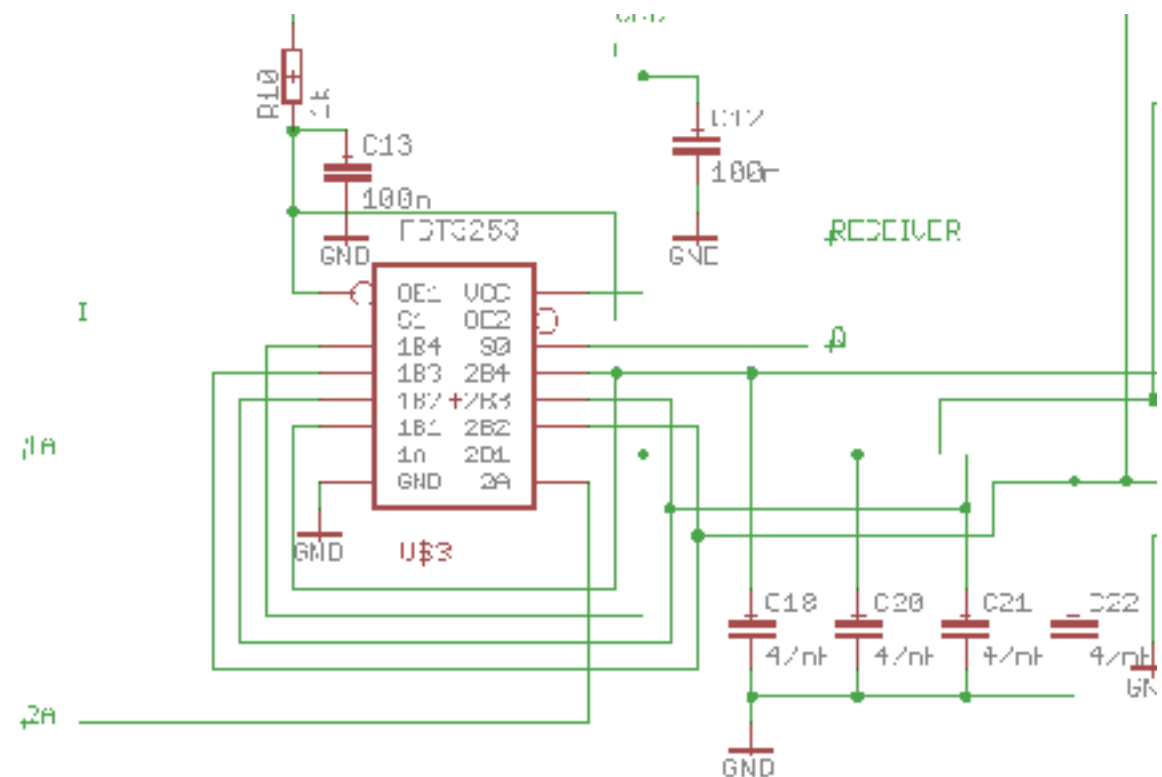

Circuit details

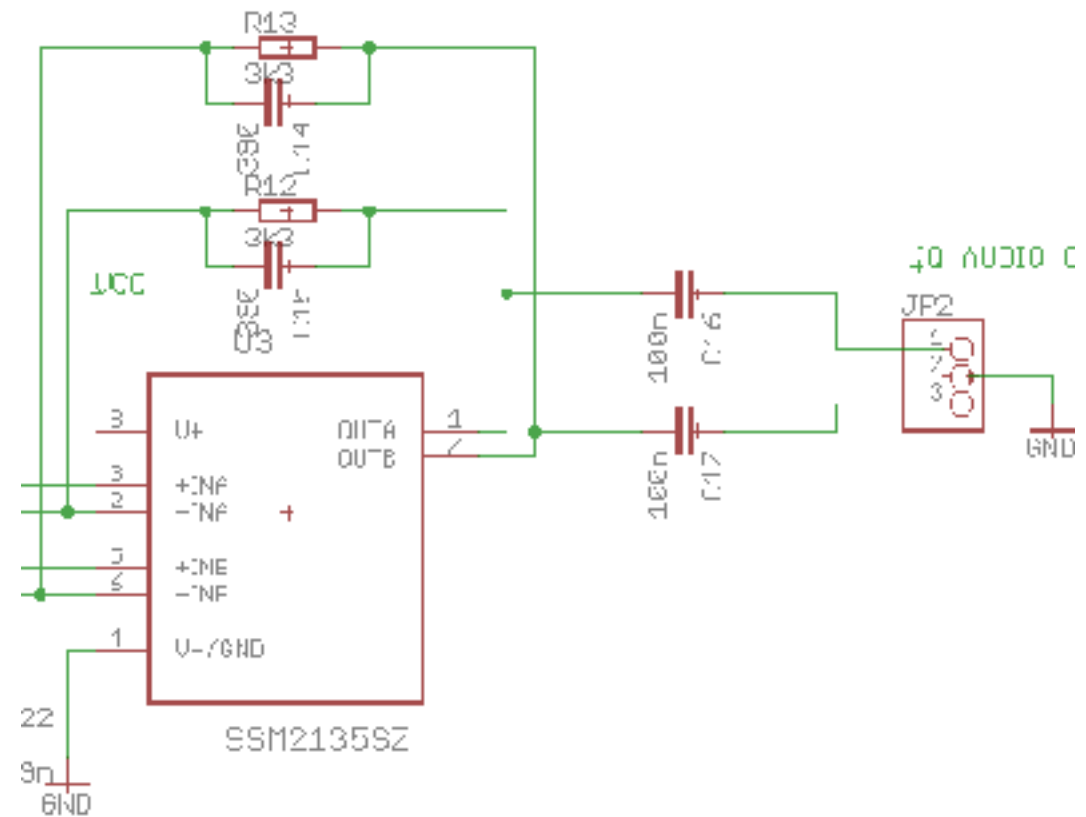- RX op-amps
- 0-180-90-270deg inputs
- I&Q audio outputs
- $3k3/100 = \times 330$ gain (50dB)



Status

- Verifying schematic, de-coupling etc
- PCB layout done, to be checked

