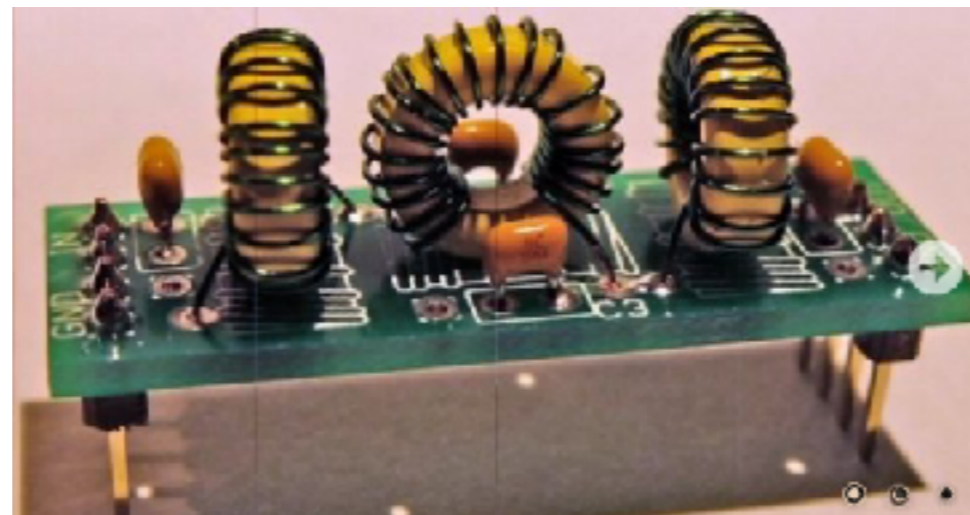


Coils, Caps Matching and Filters

Antony M0IFA



QRP-Labs LPFs \$4.60

Coils and Caps

$$Q = XL / R$$


ESR = Effective Serial
Resistance

$$Q = XC / ESR$$


$$XL = 2 * \pi * L$$

$$XC = 1 / (2 * \pi * C)$$

Coil

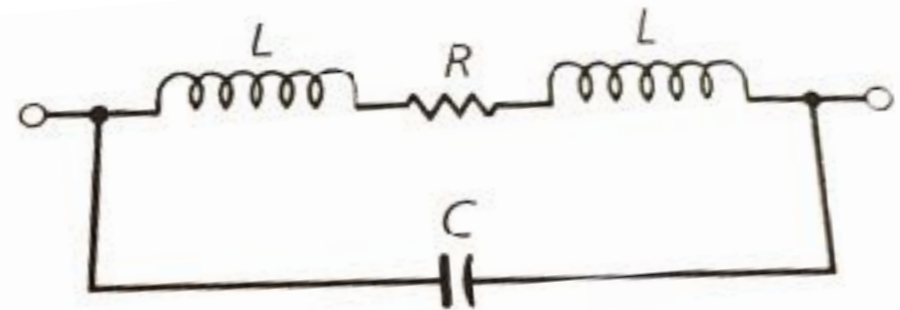

Cap

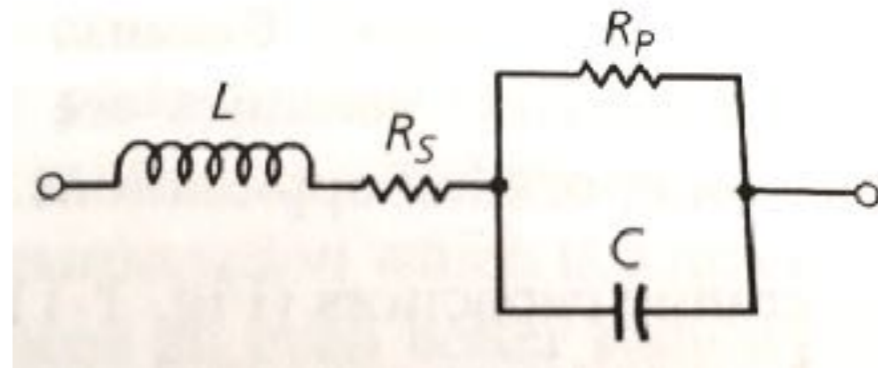

Stray Cap & Ind = self resonance

Heads-up XL & XC

Ohms

	80	40	20
1uH	22	44	88
10uH	220	440	880
100pF	450	230	114
1000pF	45	23	11
100nF	0.45	0.22	0.11

CIRCUITS





$$X_C = 1 / (2 * \pi * f)$$

$$X_L = 2 * \pi * f$$

$$X = X_C * X_L / (X_C + X_L)$$

High R_s = High Q

Add output R_l = lower Q

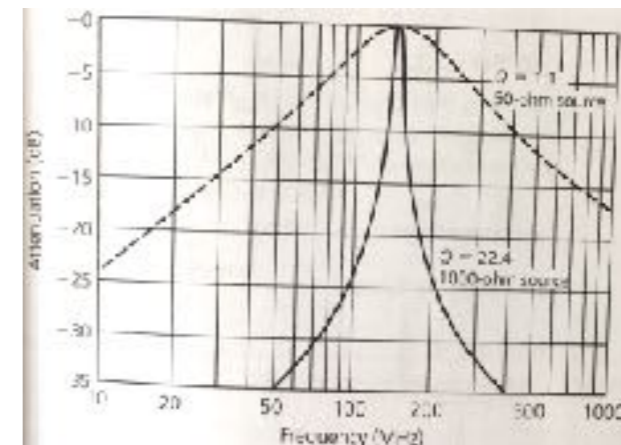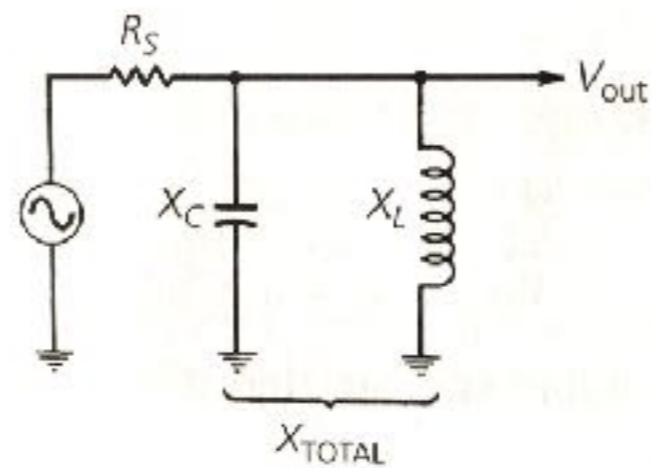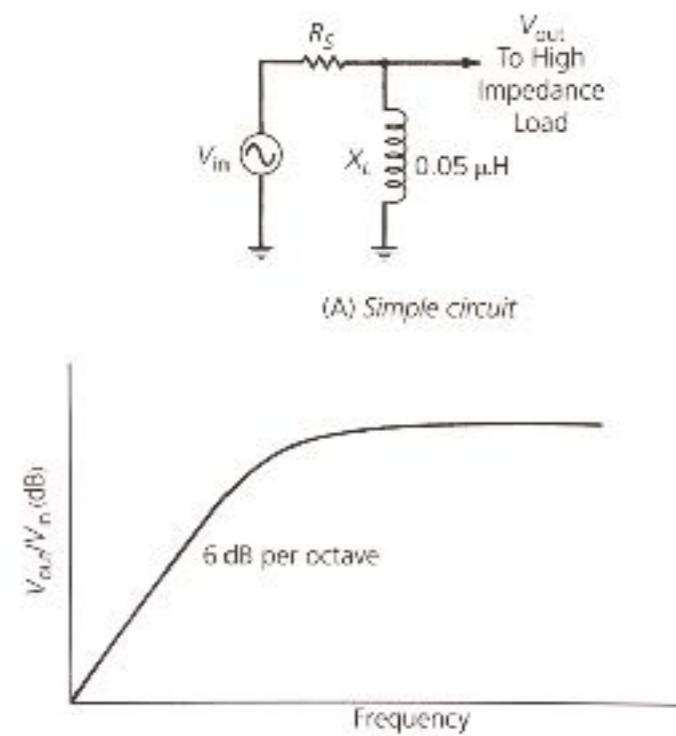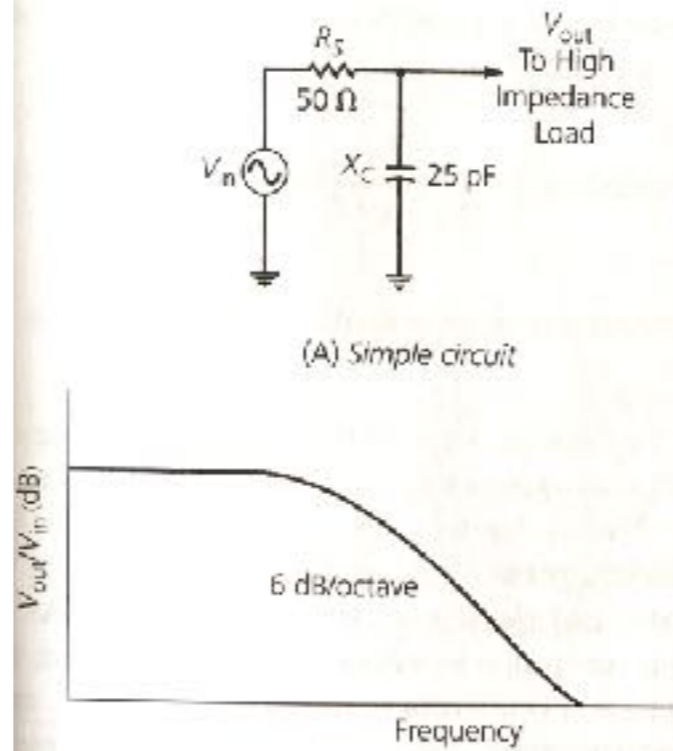


CIRCUITS


The source and load resistors
act in parallel on the circuit
and affect the Q

$$R_p = R_s * R_L / (R_s + R_L)$$

$$Q = R_p / X_c = X_l / R_p$$

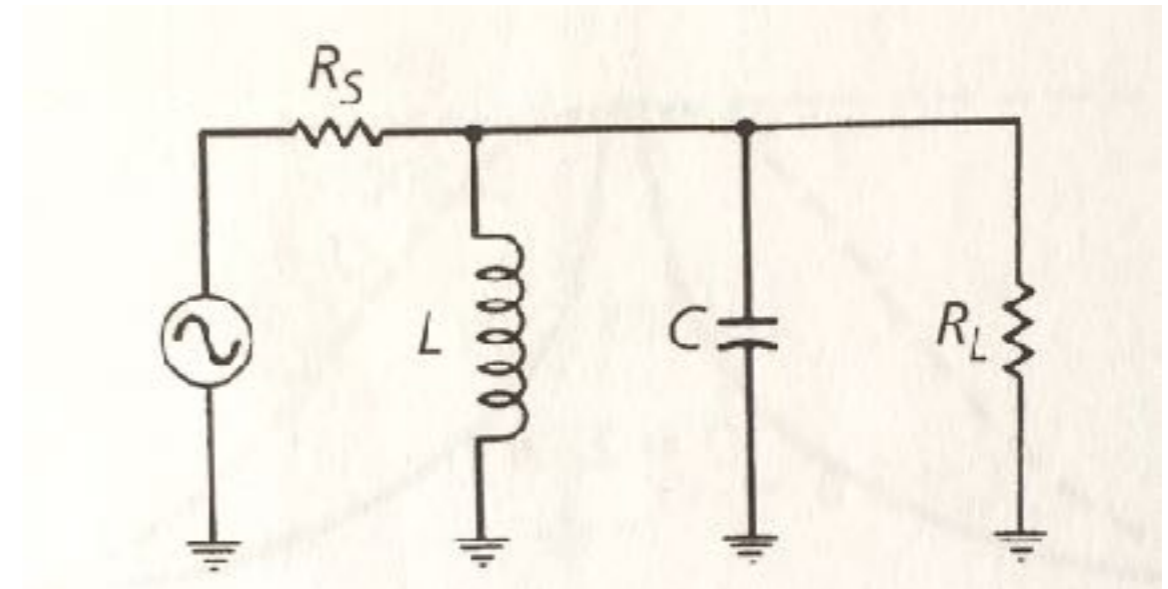

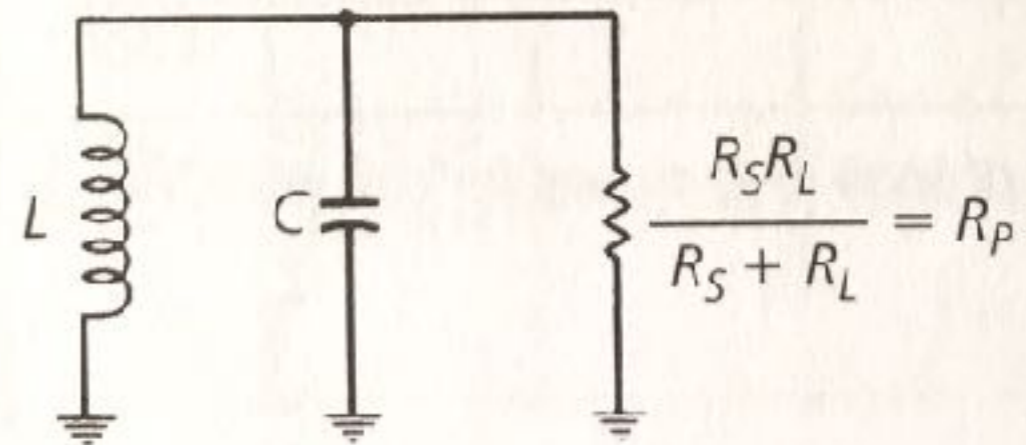
(A) Resonant circuit with an external load



(B) Equivalent circuit for Q calculations

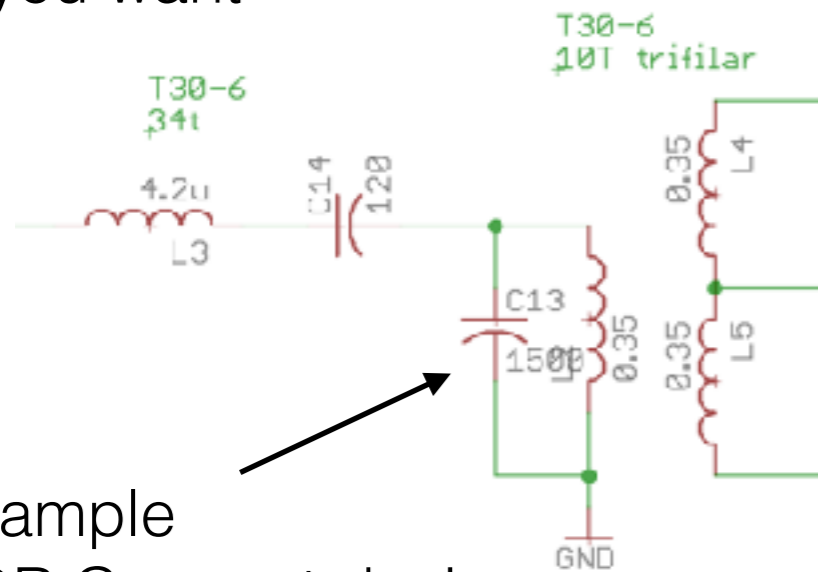
Example

You can select the values of L & C to get the response curve you want




Example
SDR Concept design
Uses High Cap & Low Ind
To get high Q
at low impedance

$Q \approx 1.1, f = 142.35 \text{ MHz}$

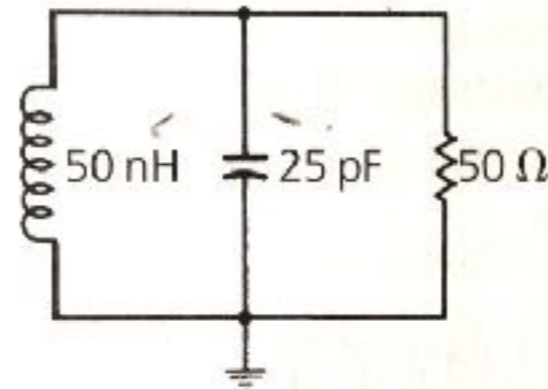


(A) Large inductor,
small capacitor

$Q \approx 22.4, f = 142.35 \text{ MHz}$

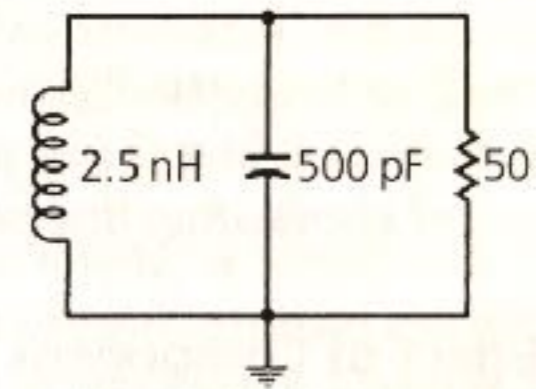

(B) Small inductor,
large capacitor


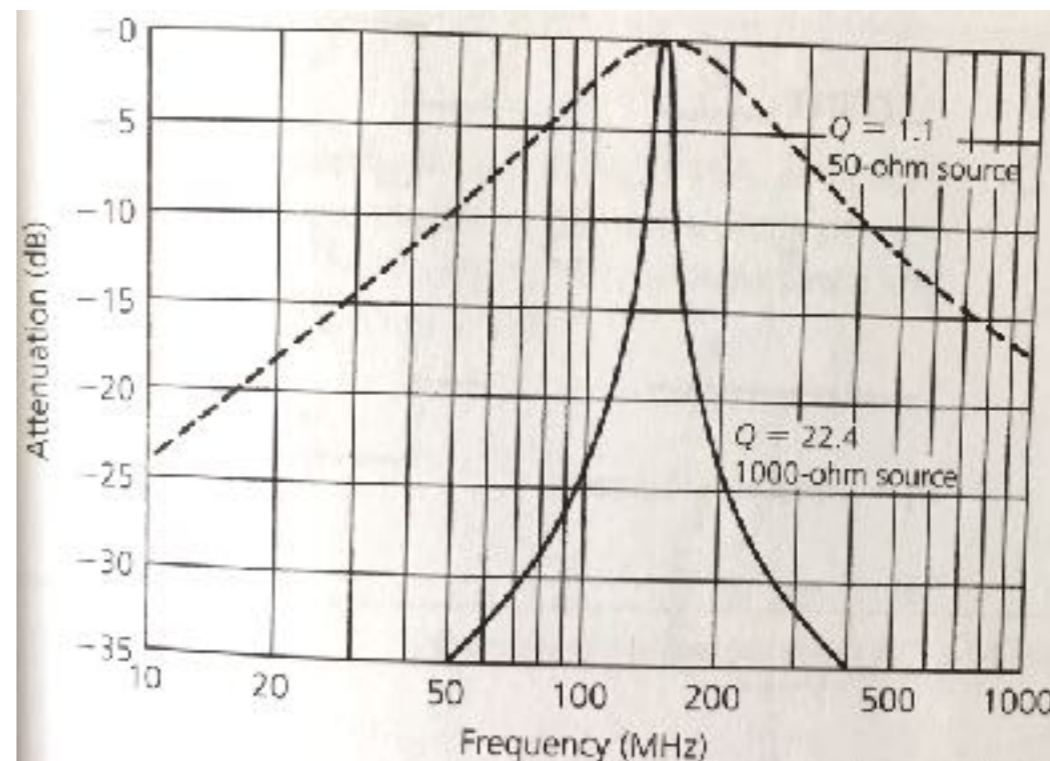


Example

You can split the capacitors into two to get the matching and Q you want

E.G to match 50R input to 1k5 input of SA612 mixer IC

As I did for my DCRX 40m design

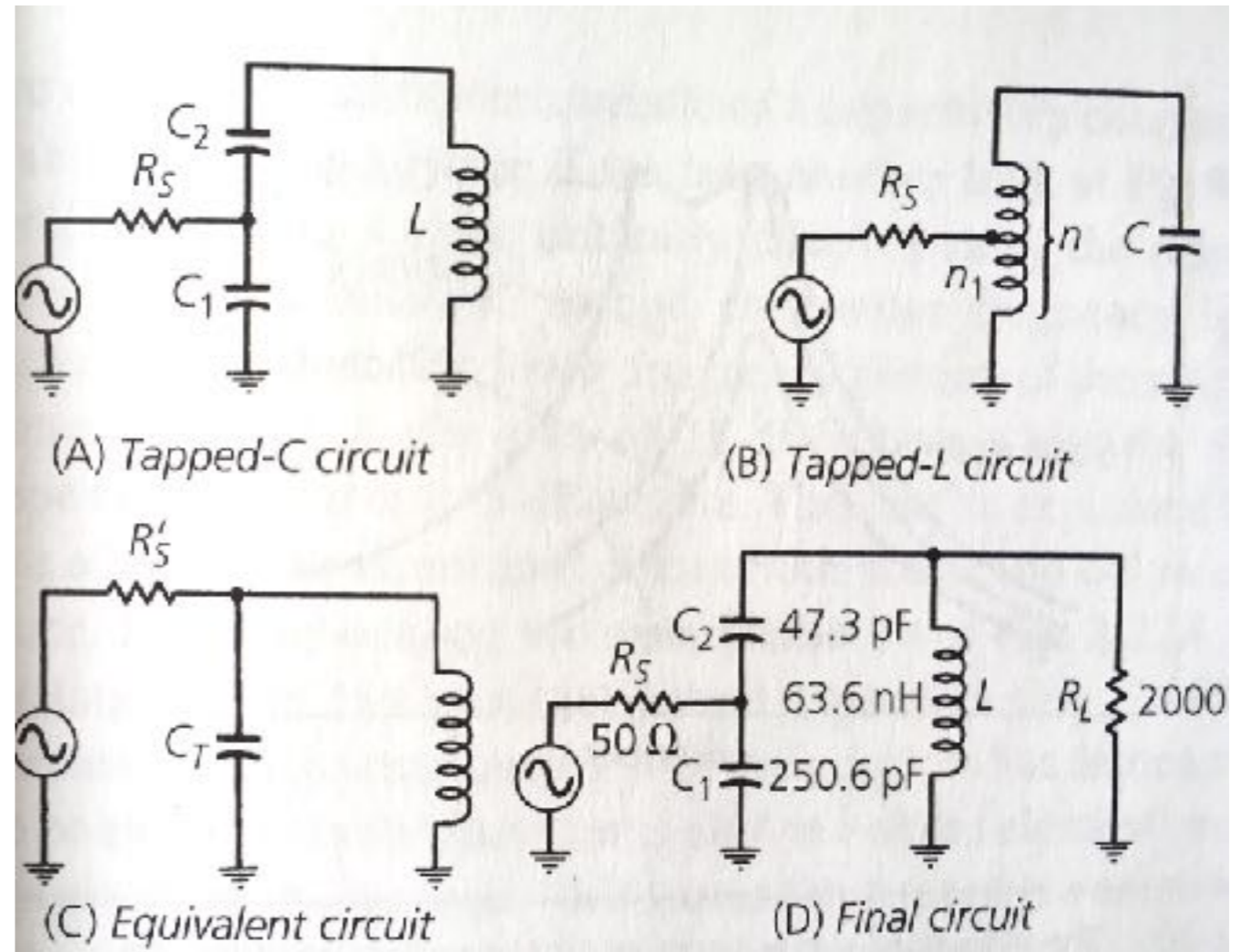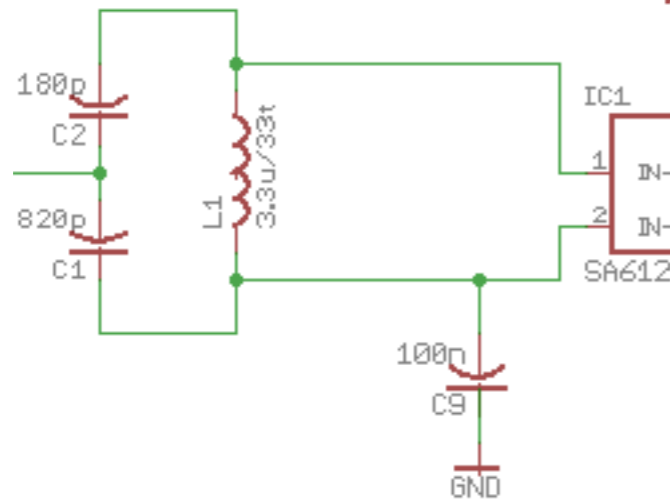

Example


Coupled tuned circuits give various responses

Depends on the coupling cap C_{12}



Big = Over coupled

Small = under coupled

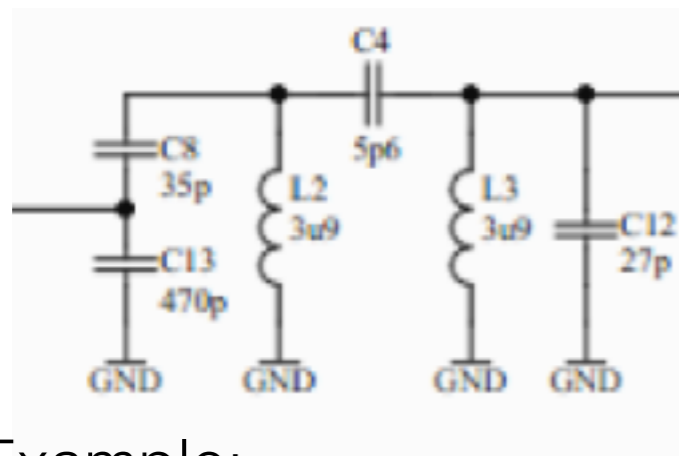Often used slightly over-coupled to give bandpass response




Example:
two techniques combined

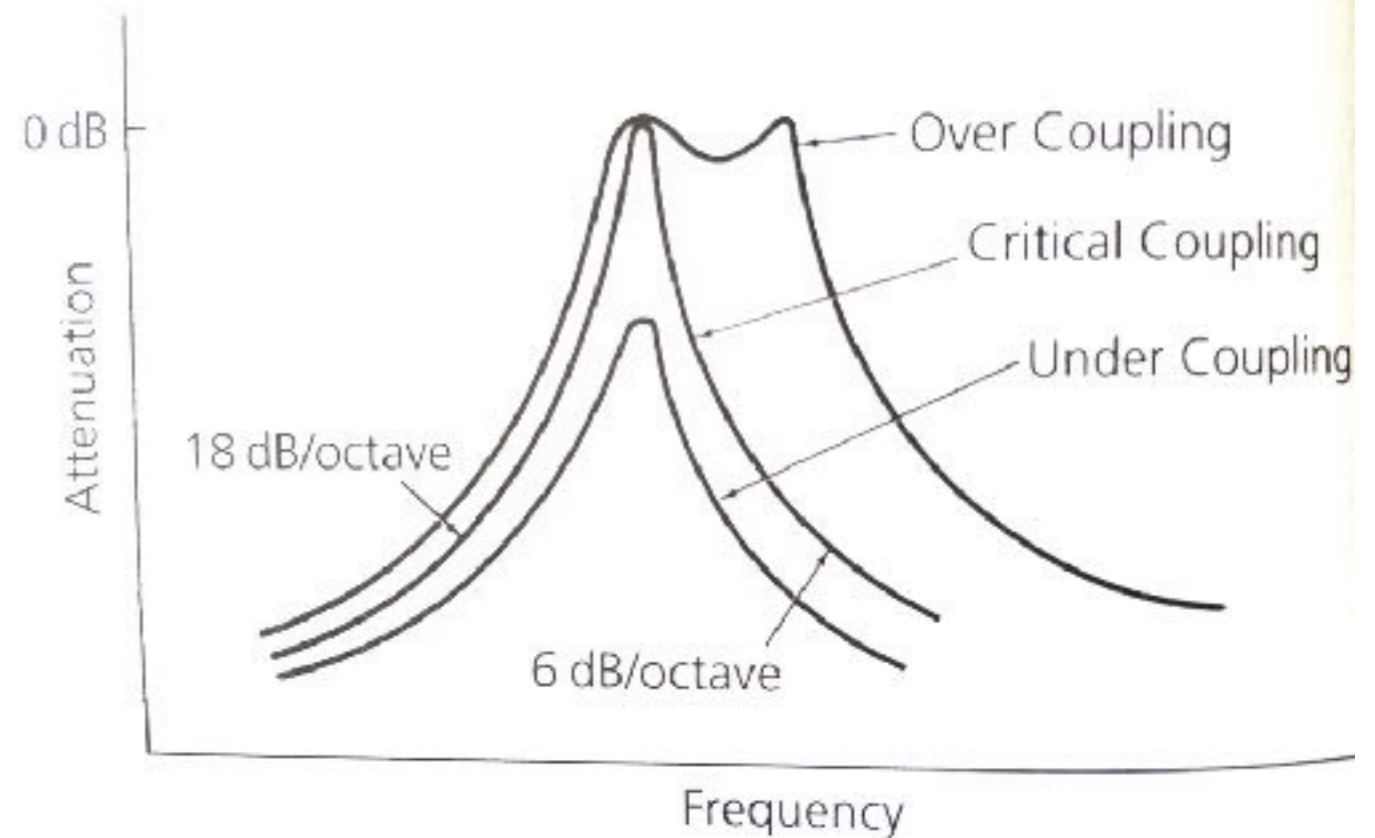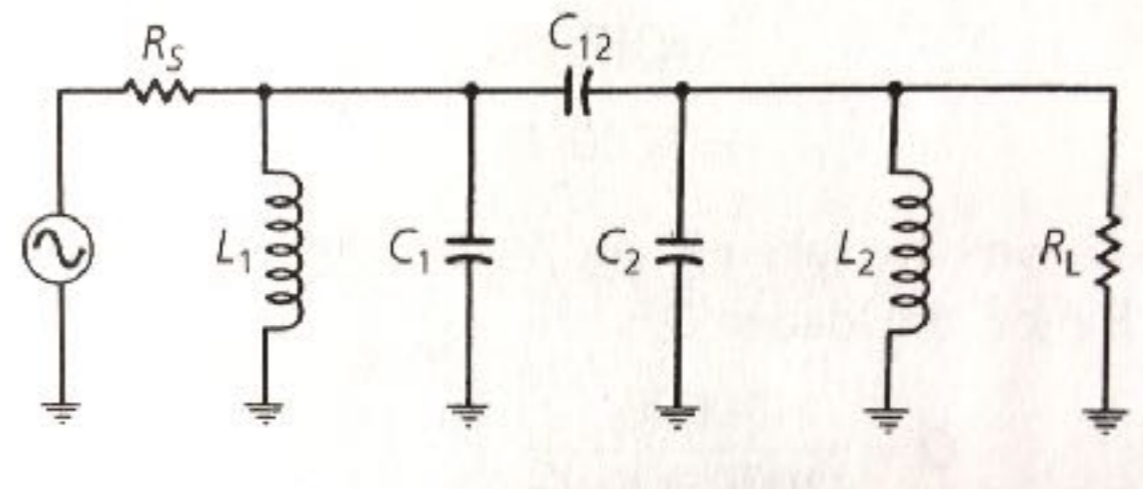

MATCHING


Maximum Power transferred
when

$$R_{\text{load}} = R_{\text{source}}$$

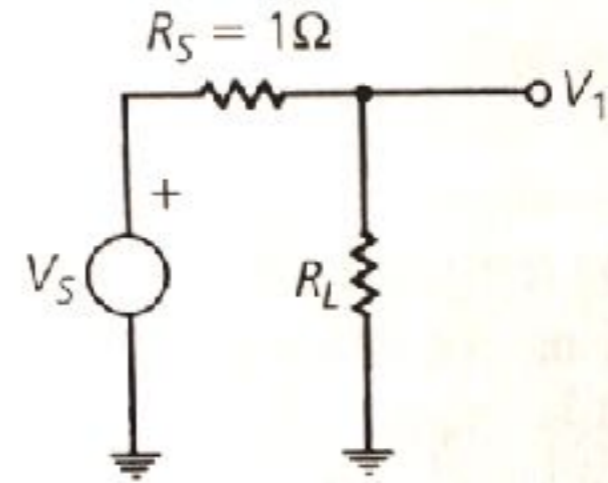

(A) Circuit

$$R_L = R_S$$

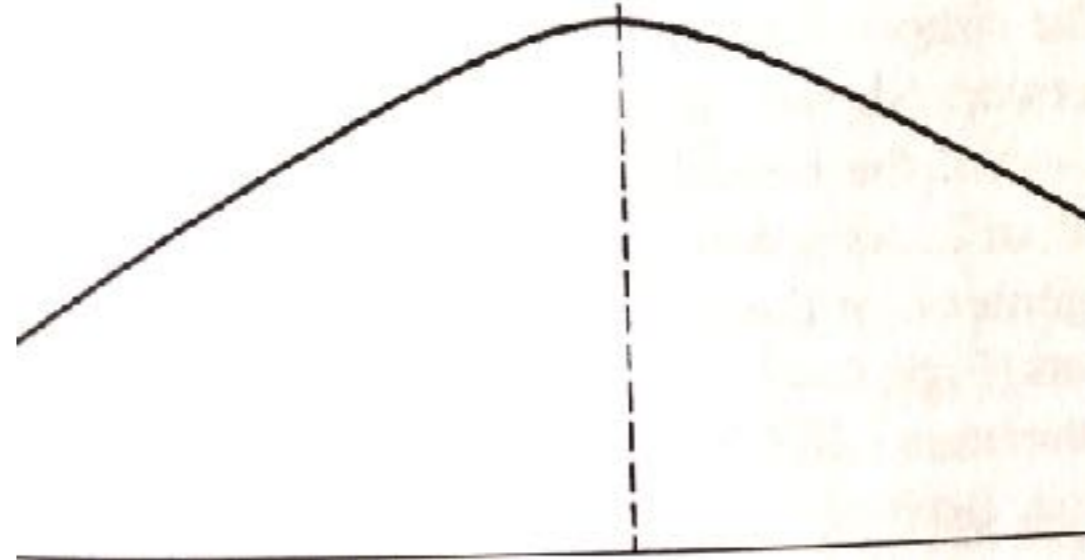

MATCHING

Four matching L networks are commonly used.

Low and High Pass

A & C


Low to High impedance

B & D

High to Low impedance

=====

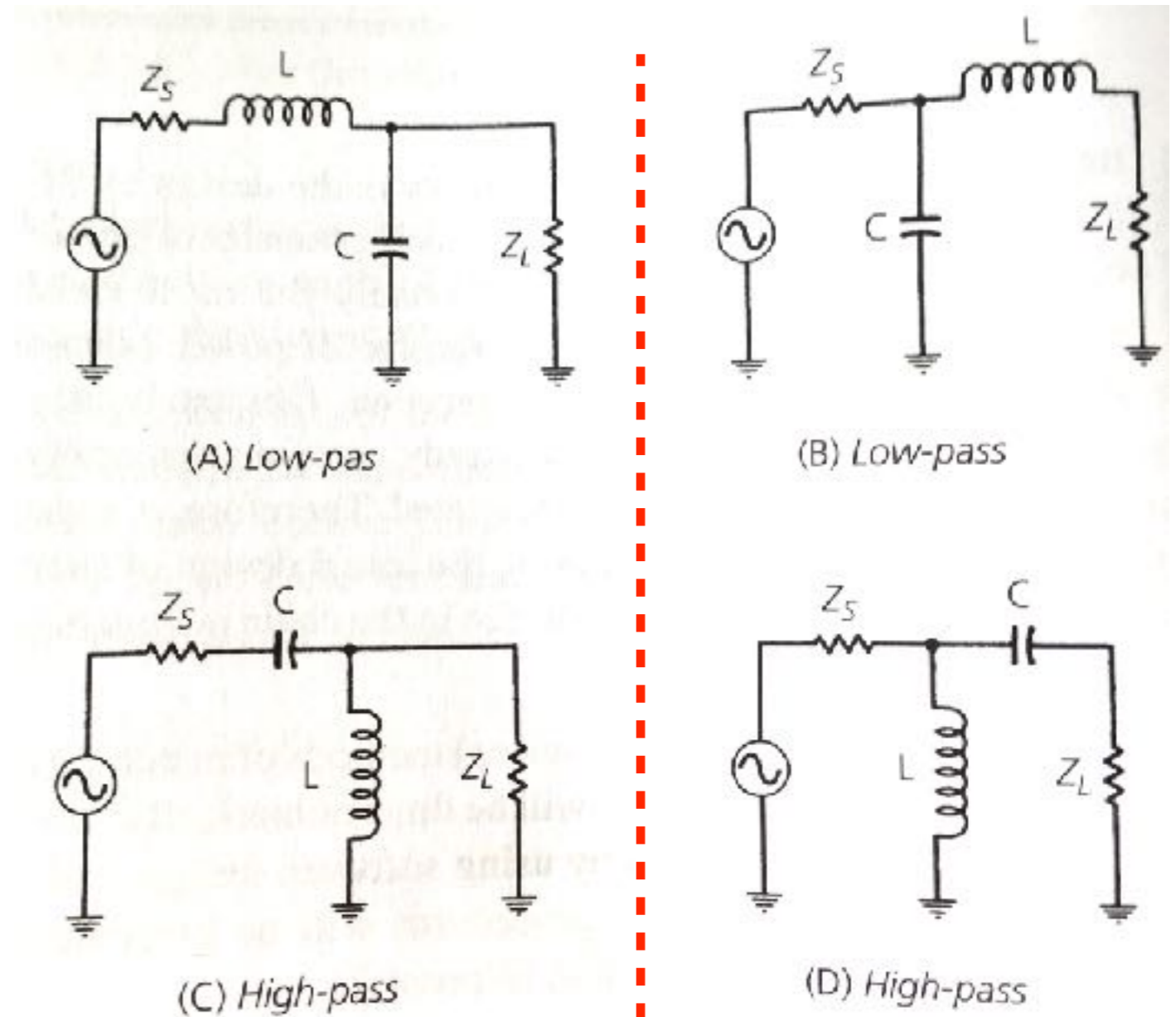These are NOT wide band matching, for that use a transformer



FILTERS



$$f_c = 1 / 2\pi\sqrt{L\cdot C}$$

$$Q_1 = X_L/R_S$$

$$Q_2 = R_L/X_C$$

$$Q = Q_1\cdot Q_2/(Q_1 + Q_2)$$

Optimum power transfer
when $Q_1 = Q_2$

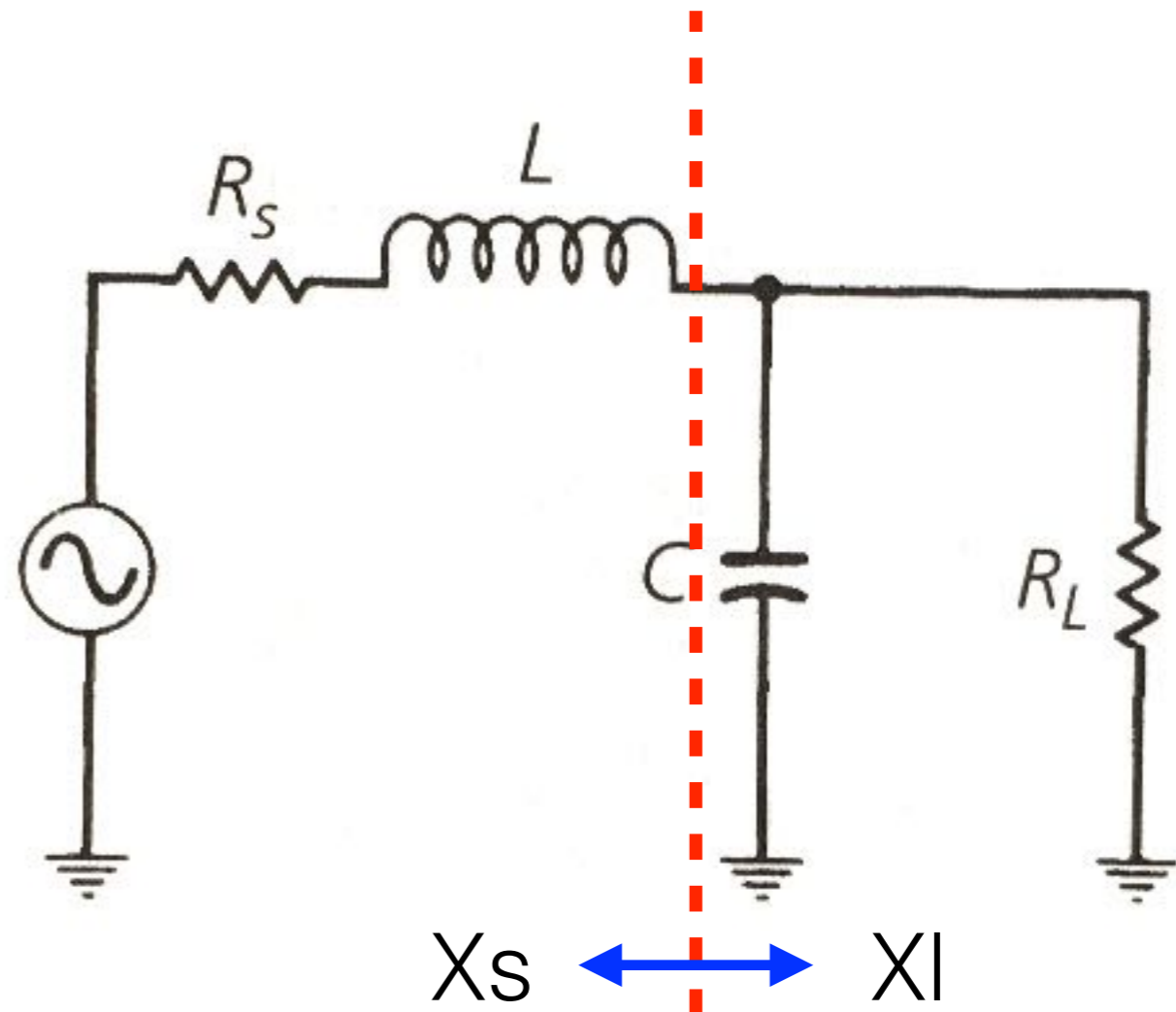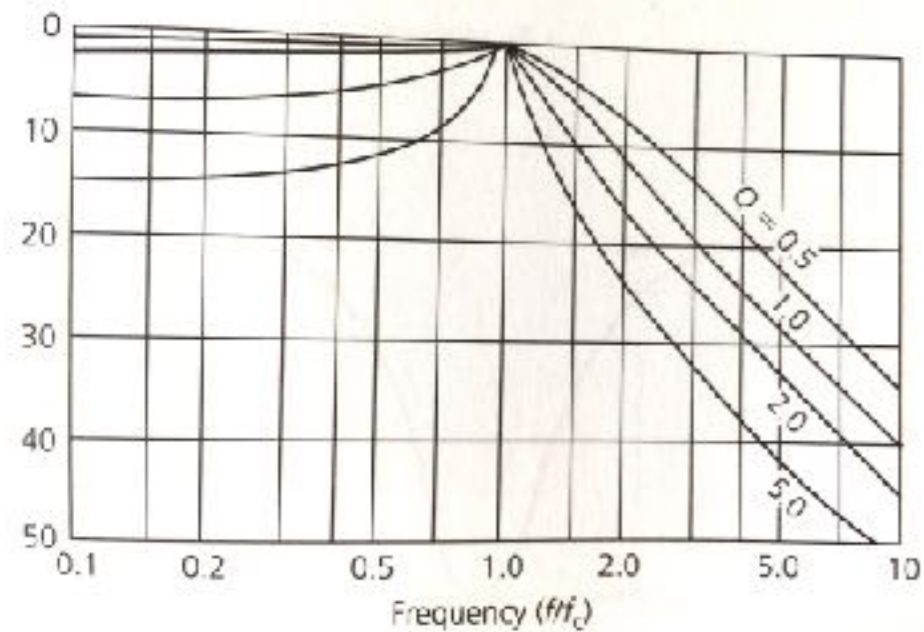



LPF

Effectively is 2 filters, joined


Filter design can have
RS different from RL

Ripple in the response

No. of peaks = No. of elements - 1

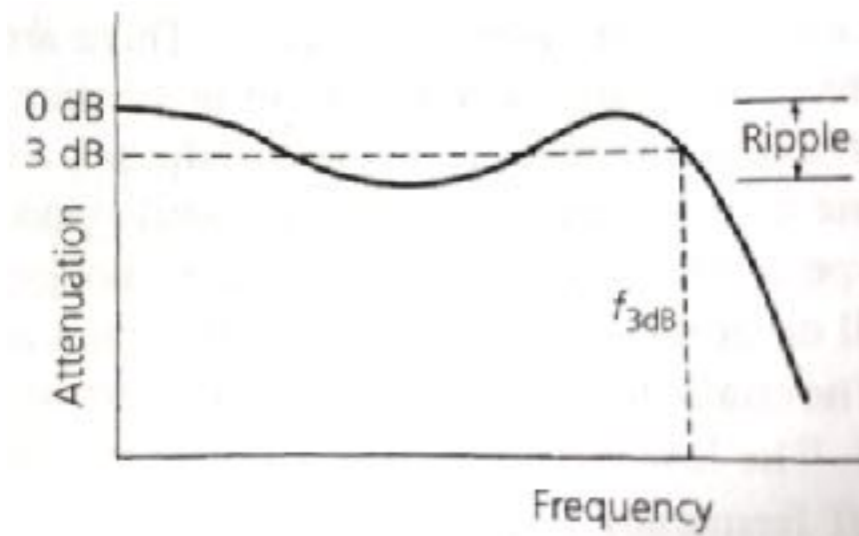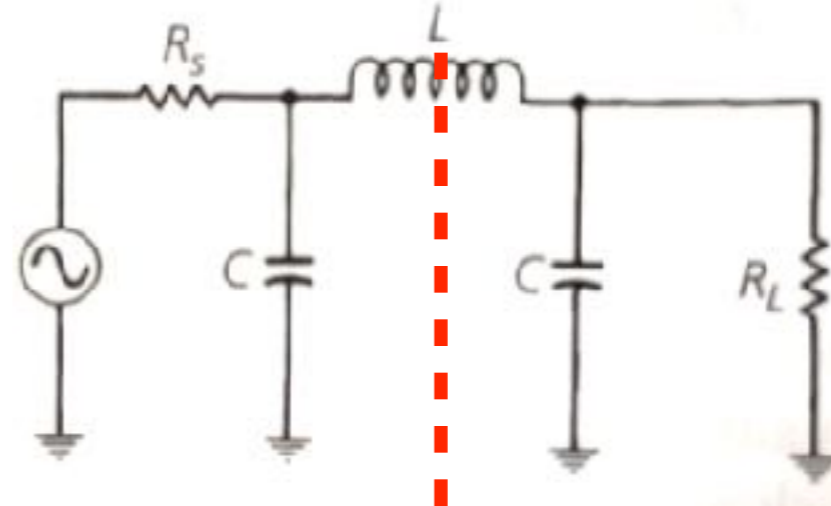

3 element LPF

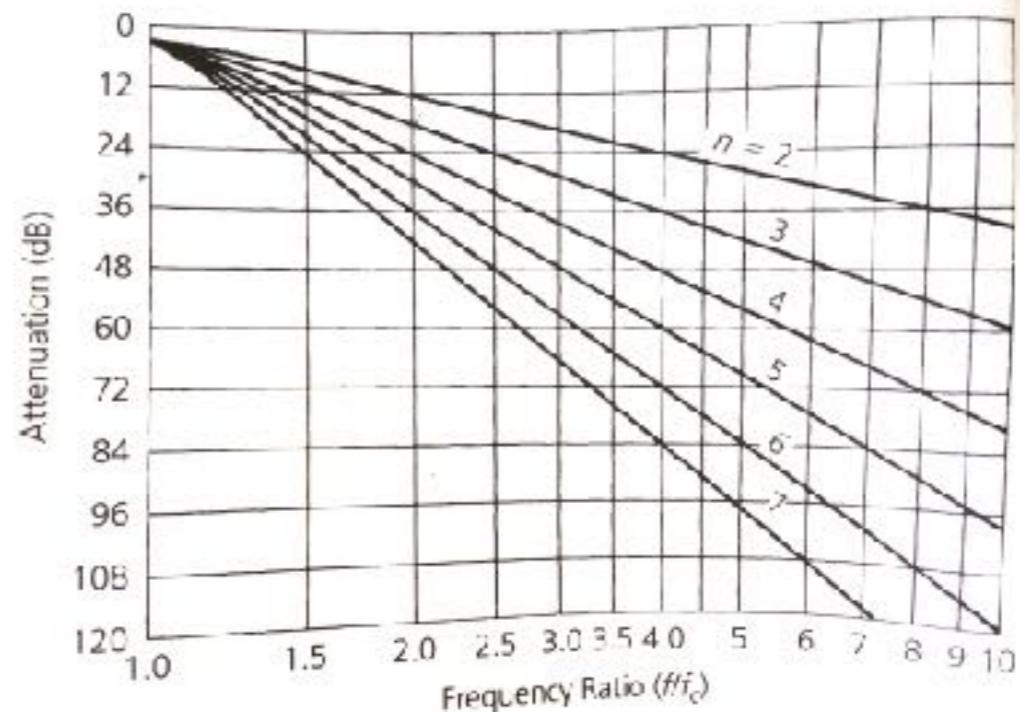

No. elements vs. Attenuation

